

Digital Computer Design

Project 1 ALU Design

Project 1.D ALU-2

1- Create the following files fulladder.sv, NbitFulladder.sv, MUX2.sv and MUX4.sv.

```
module fulladder(input logic a, b, cin,  
output logic s, cout);
```

```
    logic p, g;  
    assign p = a ^ b;  
    assign g = a & b;  
    assign s = p ^ cin;  
    assign cout = g | (p & cin);
```

```
endmodule
```


fulladder.sv

```
module NbitFulladder( input logic [3:0] a, b,  
input logic cin,  
output logic [3:0] s,  
output logic cout );
```

```
    wire [2:0] c;  
    fulladder i_0 (a[0],b[0],cin,s[0],c[0]);  
    fulladder i_1 (a[1],b[1],c[0],s[1],c[1]);  
    fulladder i_2 (a[2],b[2],c[1],s[2],c[2]);  
    fulladder i_3 (a[3],b[3],c[2],s[3],cout);
```

```
endmodule
```

NbitFulladder.sv

 

4-bit full adder using 1-bit full adders

```

module MUX2(input logic [3:0] d0, d1,
            input logic s,
            output logic [3:0] y);

    assign y = s ? d1 : d0;

endmodule

```

MUX2.sv

```

Module MUX4(input logic [3:0] d0, d1, d2, d3,
            input logic [1:0] s,
            output logic [3:0] y);

    assign y = s[1] ?
        (s[0] ? d3 : d2):
        (s[0] ? d1 : d0);

endmodule

```

MUX4.sv

